
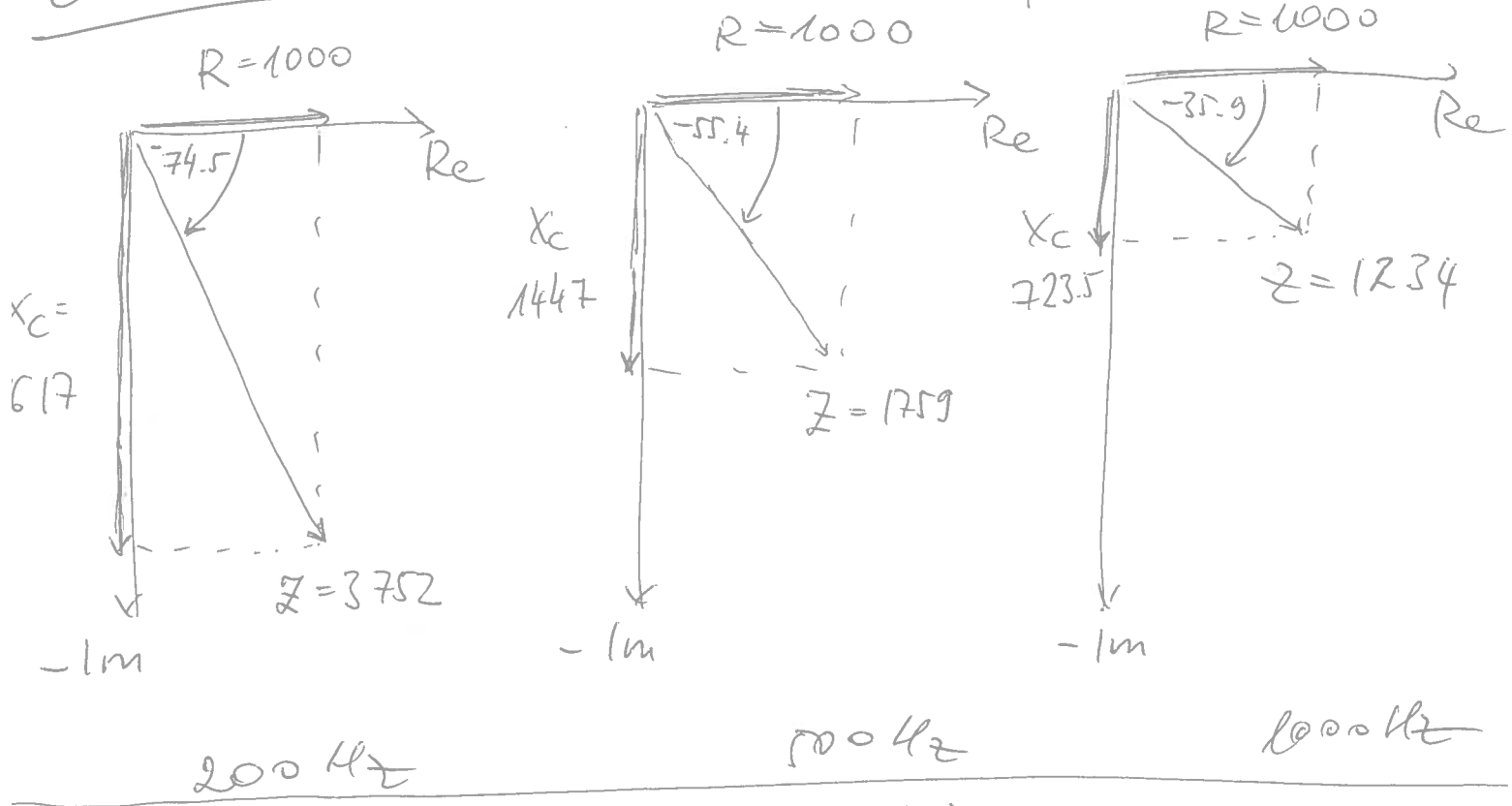


$f$	$X_c$	$R$	$V_r = 5 \cdot \frac{R}{ Z }$	$V_c = 5 \cdot \frac{X_c}{ Z }$	$\varphi$
200 Hz	3617 $\Omega$	1000 $\Omega$	1.33 V	4.82 V	-74.5°
500 Hz	1447 $\Omega$	1000 $\Omega$	2.84 V	4.11 V	-55.4°
1000 Hz	723.5 $\Omega$	1000 $\Omega$	4.05 V	2.93 V	-35.9°

Circuit 1.

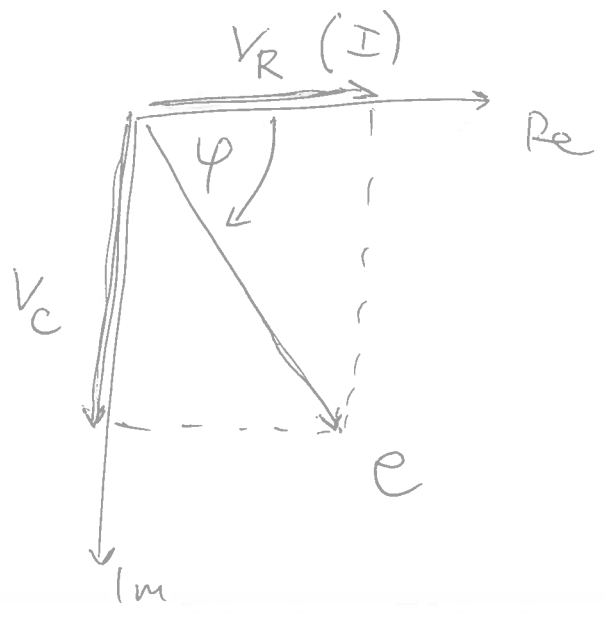

measurement:



## Circuit 2

In theory, the resonance frequency is approx.

500 Hz for the given values, but I got maximal

$V_r$  @ 475 Hz.

Due to the internal resistance  $\approx 70 \Omega$  of  $L$ ,  
the maximum of  $V_r$  is:



$$(V_r)_{\max} = 5 \cdot \frac{470}{470 + 70} \approx 4.35 \text{ V}$$

Similarly the  $\omega_{\text{low}}$  and  $\omega_{\text{HIGH}}$  values are also  
affected by  $R_{\text{internal}}$ .

$$\omega_{1,2} = \frac{\sqrt{R^2 + \frac{4L}{C}} \pm R}{2L} \quad \left\{ \begin{array}{l} \sim 232.1 \text{ Hz}, 1458 \frac{\text{rad}}{\text{s}} \\ \sim 1091.5 \text{ Hz}, 6858 \frac{\text{rad}}{\text{s}} \end{array} \right.$$

But  $\omega_{\text{low}} \cdot \omega_{\text{HIGH}} \equiv \omega_{\text{res}}^2$  should be true.

frequency [Hz]	$e_{\text{RMS}}$ [V]	$V_r$ [V] RMS	$V_L$ [V] RMS	$V_C$ [V] RMS	$R$ [ $\Omega$ ]	$X_L$ [ $\Omega$ ]	$X_C$ [ $\Omega$ ]	$\varphi$
232.1	5	3.05	0.955 1.06	4.49	470	145.8	685.7	$-45^\circ$
500	5	4.35	2.91 2.98	2.95	470	314.2	318.3	$\sim 0^\circ$
1091.5	5	3.05	<del>4.49</del> 4.51	0.95	470	685.8	145.8	$+45^\circ$

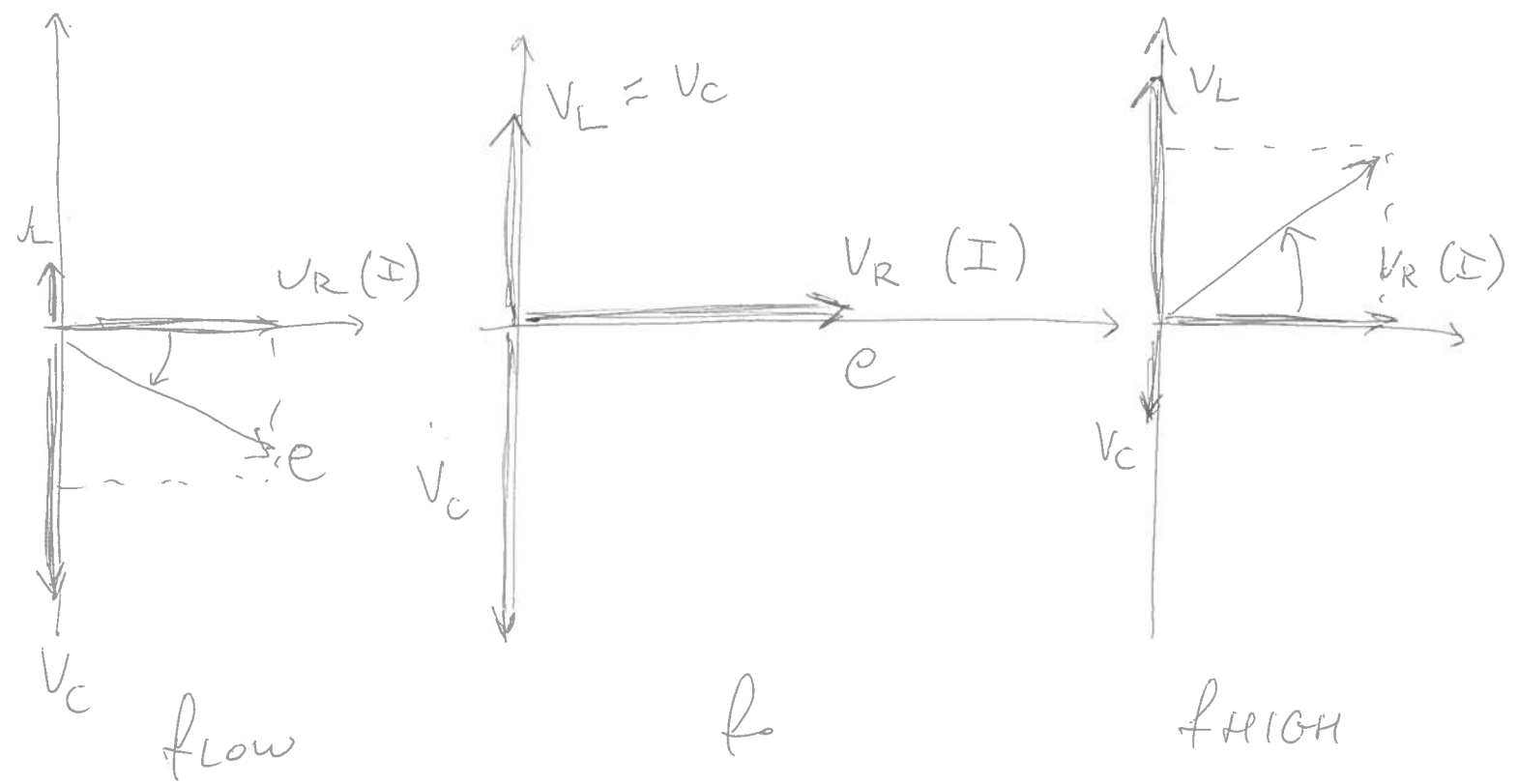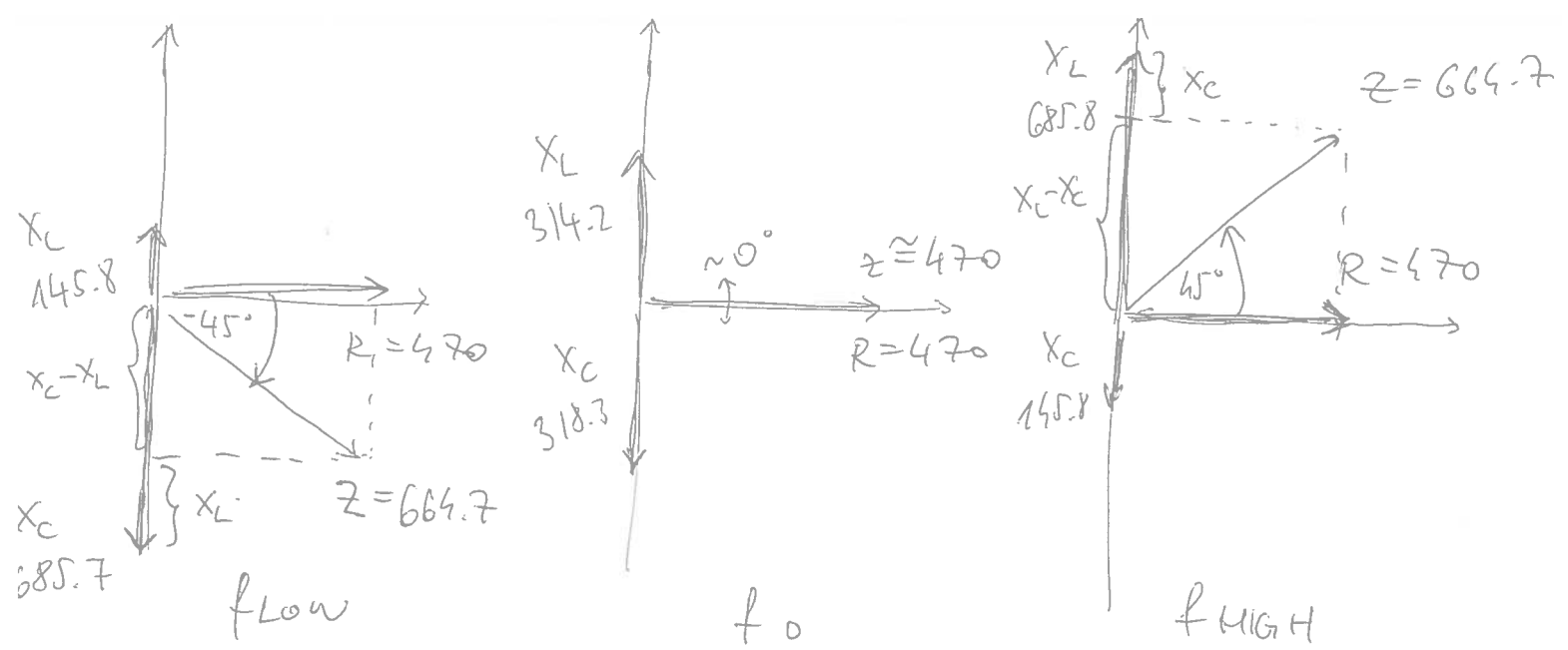

Due to  $R_{int}$  error, the angles here are  $45^\circ - 55^\circ$  instead of  $45^\circ$ .

and  $(V_L - V_C)^2 + V_R^2 \neq e$