

Circuit 31: Parallel RC

resistor	conductance G	cap.	cap. react.	cap. suscept. B	total adm.
1000Ω	1 mS	$0.22 \mu\text{F}$	-1447Ω	0.7 mS	$1.22 \angle 35^\circ \text{ mS}$

capacitor current:

$$|i_C| = \frac{5}{1447} = 3.46 \text{ mA} (= 5 \text{ V} \times 0.7 \text{ mS})$$


resistor current:

$$|i_R| = \frac{5}{1000} = 5 \text{ mA} (= 5 \text{ V} \times 1 \text{ mS})$$


total current:

$$i_T = 5 \cdot (1 \text{ mS} + 0.7j \text{ mS}) = 5 + 3.46j \text{ mA} = 6.08 \angle 35^\circ \text{ mA}$$

phasor diagram

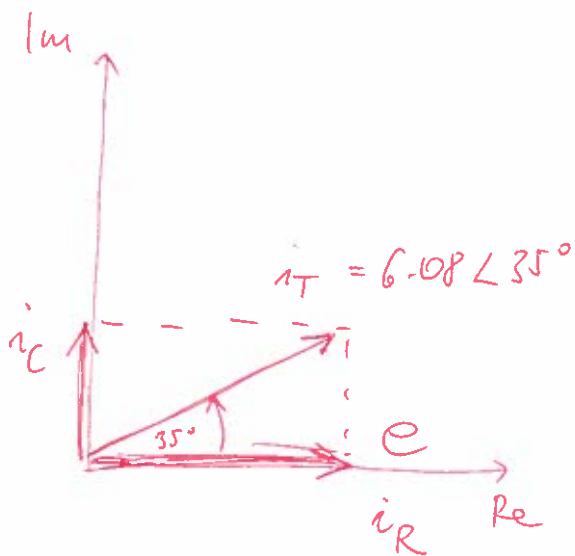

admittance diagram

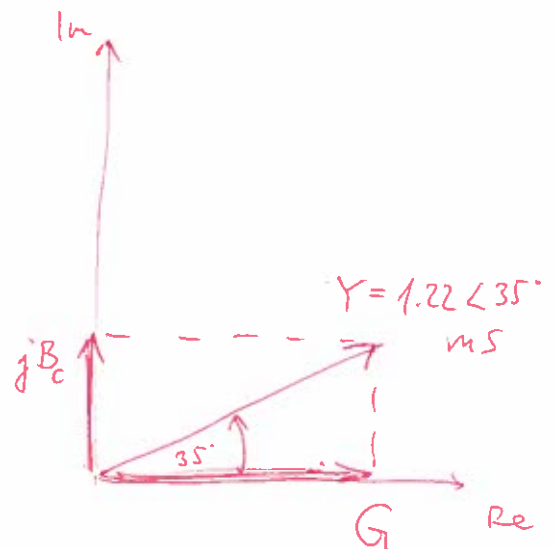

Circuit B2: parallel LC

a) $X_L = \omega L$ $|i_L| = \frac{e}{X_L}$ For given values $|i_L| \approx 8 \text{ mA}$
 (this will be measured)
 $L = 100 \text{ mH}$

b) $i_C = i_e \cdot \frac{z_L}{z_L + z_C} = i_e \cdot \frac{j\omega L}{j\omega L - j\frac{1}{\omega C}} = -0.65 \cdot i_e \quad (+90^\circ \text{ w.r.t. } e)$
 (re measured)


$i_L = i_e \cdot \frac{z_C}{z_C + z_L} = 1.65 \cdot i_e$

c) V_R is known $\rightarrow i_R = \frac{V_R}{100 \Omega} \equiv i_C$ compare with above
 (measured)

d) $Y = j\omega C - j\frac{1}{\omega L} = -0.964 j \mu\text{S}$ (neglecting R)

$i_e = \frac{e}{Z} = e \cdot Y = -4.82 j \text{ mA}$

Phasor diagram

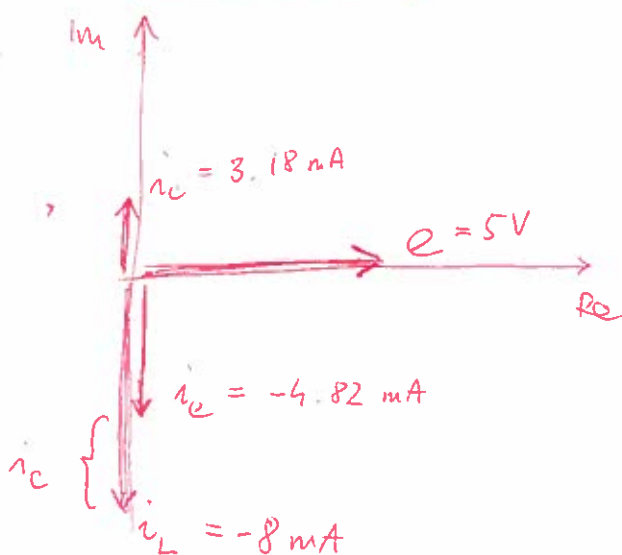

Admittance diagram

