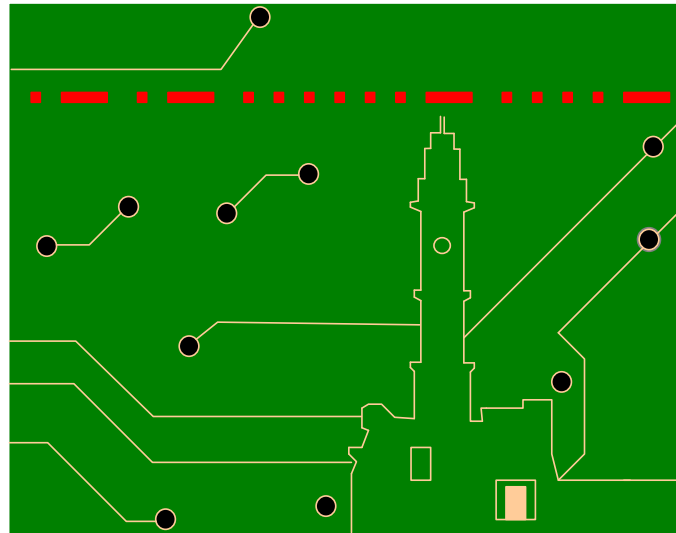


ΤΗΛ412 Ανάλυση & Σχεδίαση (Σύνθεση) Τηλεπικοινωνιακών Διατάξεων


Διάλεξη 6



Άγγελος Μπλέτσας

ΗΜΜΥ Πολυτεχνείου Κρήτης, Φθινόπωρο 2014

...και όμως η Γη γυρίζει...

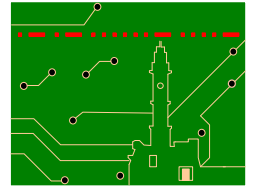

- iCubes v0.2, designed through TEL412...
- bottom line: you can do it ...

Lecture 6 – Cascaded Systems Revisited: Receiver RF Chain NF and IP3 example

Previous lecture:


- Homodyne Receiver (and disadvantages), SuperHet

Receiver, Subsampling and Digital-IF Receiver, Dynamic Range of ADC.

Today,

- Cascaded Systems, revisited:

NF and IP3 example of a RF receiver chain


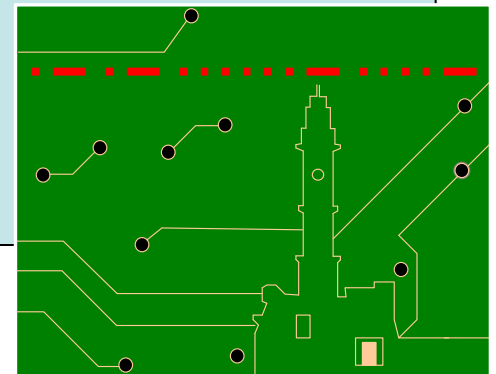


Διάλεξη 6

Figures/material for today's lecture come from:
B. Razavi, RF Microelectronics, Prentice Hall
1998.



Receiver Front End - revisited

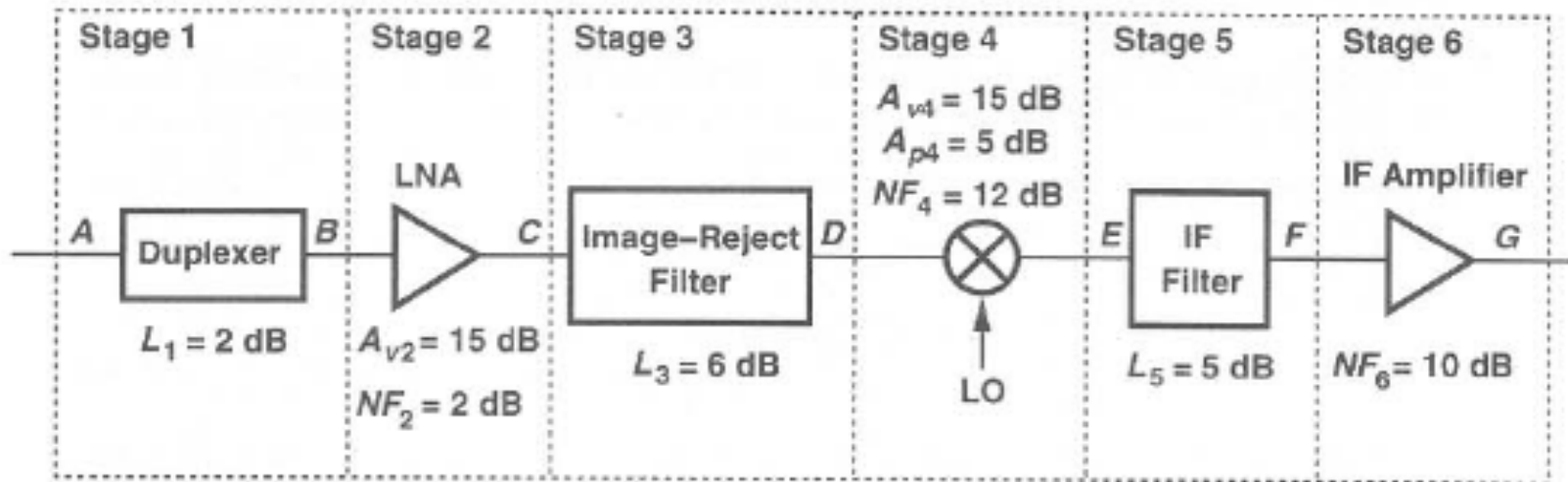
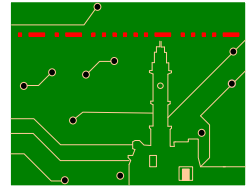


- What is the overall NF? What is the overall IP3?
- Remember that NF is referenced to a specific input resistance...
- Power Gain depends on input resistance...

$$NF_{\text{tot}} = 1 + (NF_1 - 1) + \frac{NF_2 - 1}{A_{p1}} + \dots + \frac{NF_m - 1}{A_{p1} \cdot \dots \cdot A_{p(m-1)}}$$

- Trick: to avoid confusion, convert all power gains to voltage-squared gains – the latter are R-independent!

Receiver Front End - revisited

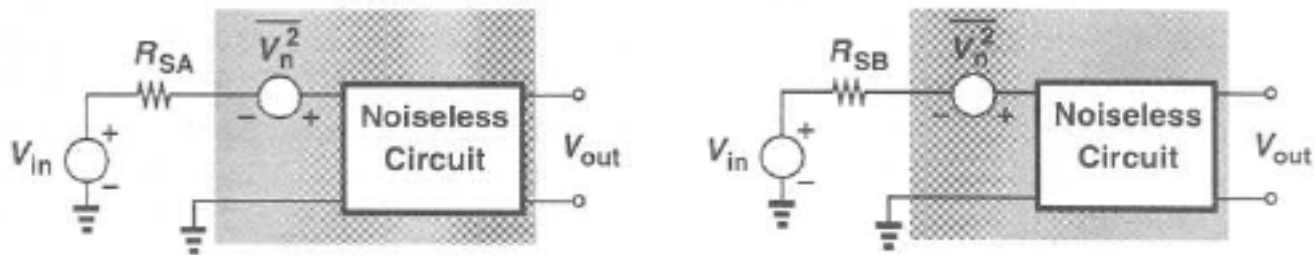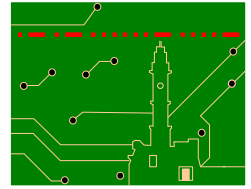



**Product is
R_S -
independent!**

- Assuming no input noise current, we have shown that:

$$\begin{aligned}
 NF_A &= 1 + v_n^2 / (4KTR_{SA}) \\
 NF_B &= 1 + v_n^2 / (4KTR_{SB})
 \end{aligned}
 \Rightarrow (NF_A - 1)R_{SA} = (NF_B - 1)R_{SB}$$

- If NF is given for a specific input resistance, other than the output resistance of the previous stage, then NF value in Friss equation is divided with voltage gain squared!

Receiver Front End - revisited

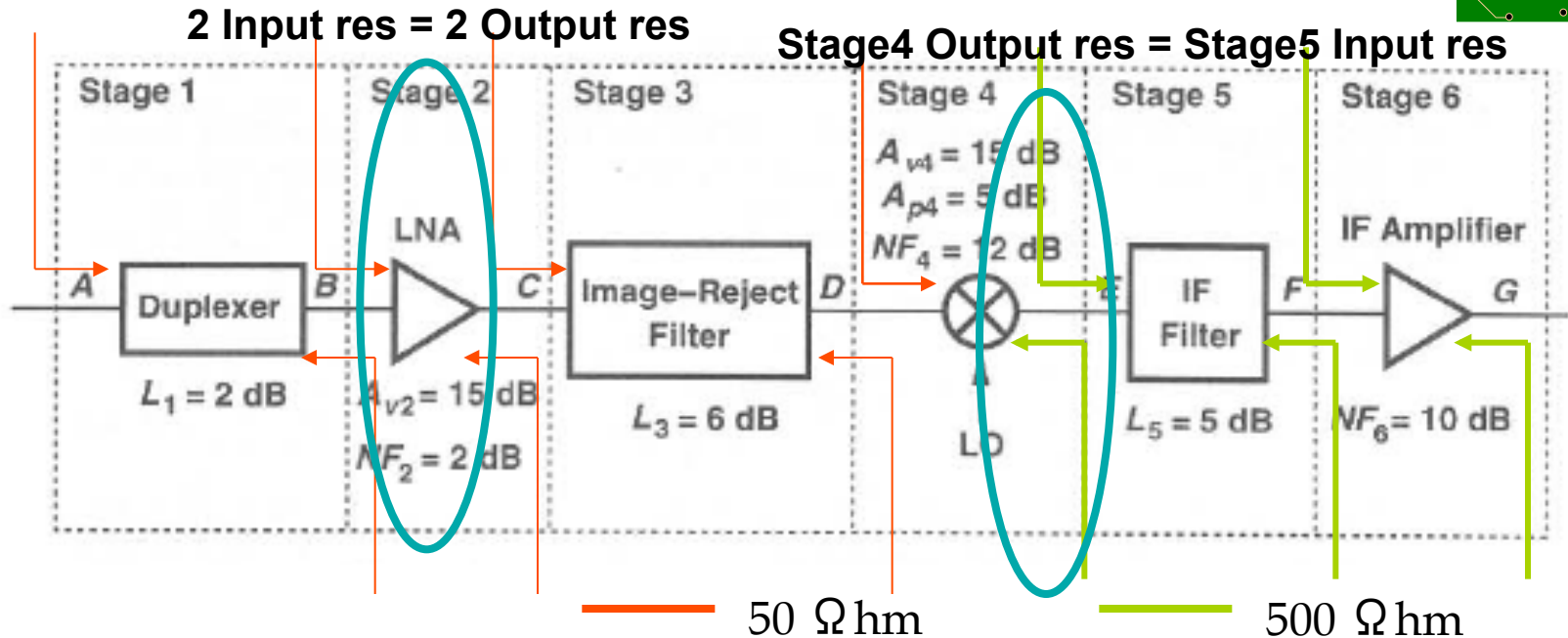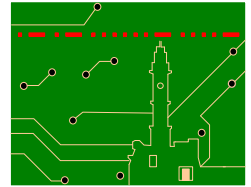

- $NF_E = L_5 NF_{LNA} \Rightarrow 5 + 10 = 15 \text{ dB} = 31.6$

(assuming $NF_6 = 10 \text{ dB}$ is referenced to 500Ω hm).



- $NF_D = NF_{LO} + (NF_E - 1)/A_{p4} = 10^{1.2} + 30.6/10^{0.5} = 15.85 + 30.6/3.16 = 25.53 = 14.1 \text{ dB}$.

- $NF_C = L_3 NF_D \Rightarrow 6 + 14.1 = 20.1 \text{ dB} \Rightarrow 102.3$.

- $NF_B = NF_2 + (NF_C - 1)/A_{v2}^2 = 10^{0.2} + 101.3/10^{1.5} = 1.58 + 3.2 = 4.78 = 6.79 \text{ dB}$



...careful!!!

Receiver Front End - revisited

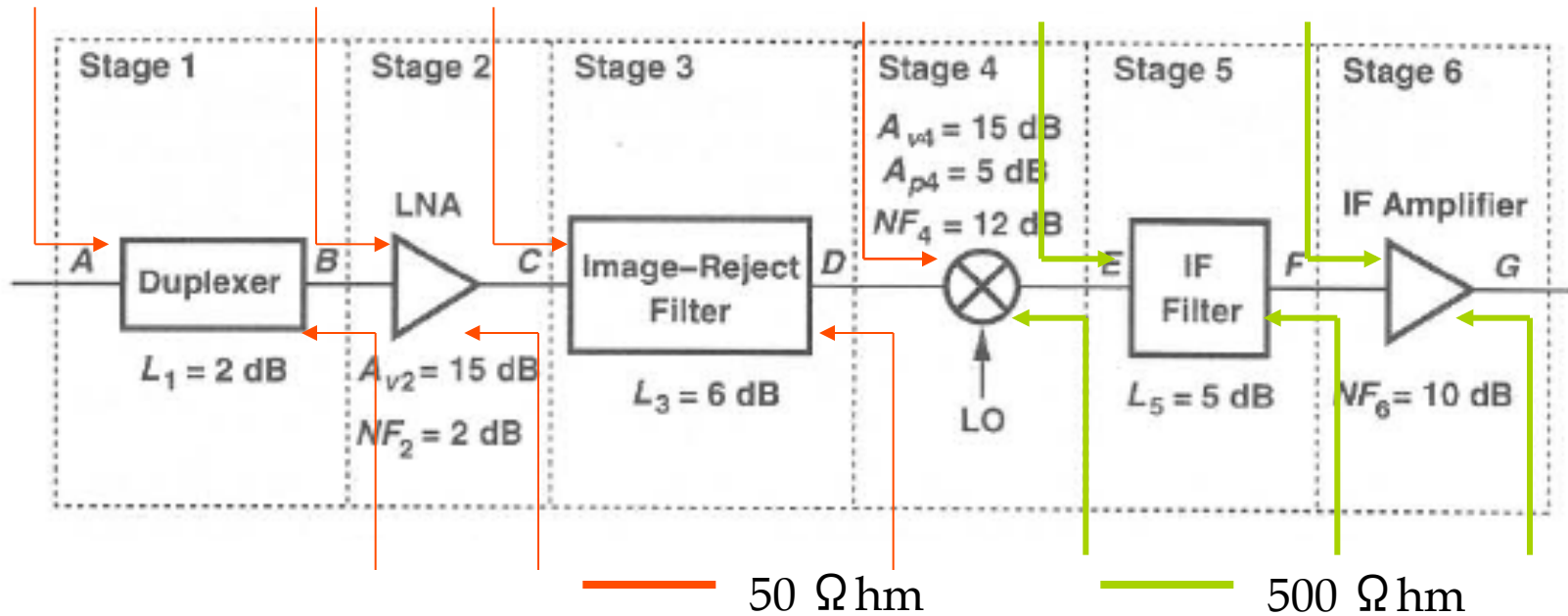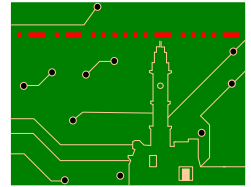

- $NF_A = L_1 + NF_B = 6.79 + 2 = 8.79 \text{ dB}$.
- Remember that $NF_C = 20.1 \text{ dB}$...
- ...confirms that initial stages of RF chain are the most NF-critical...



Receiver Front End - revisited

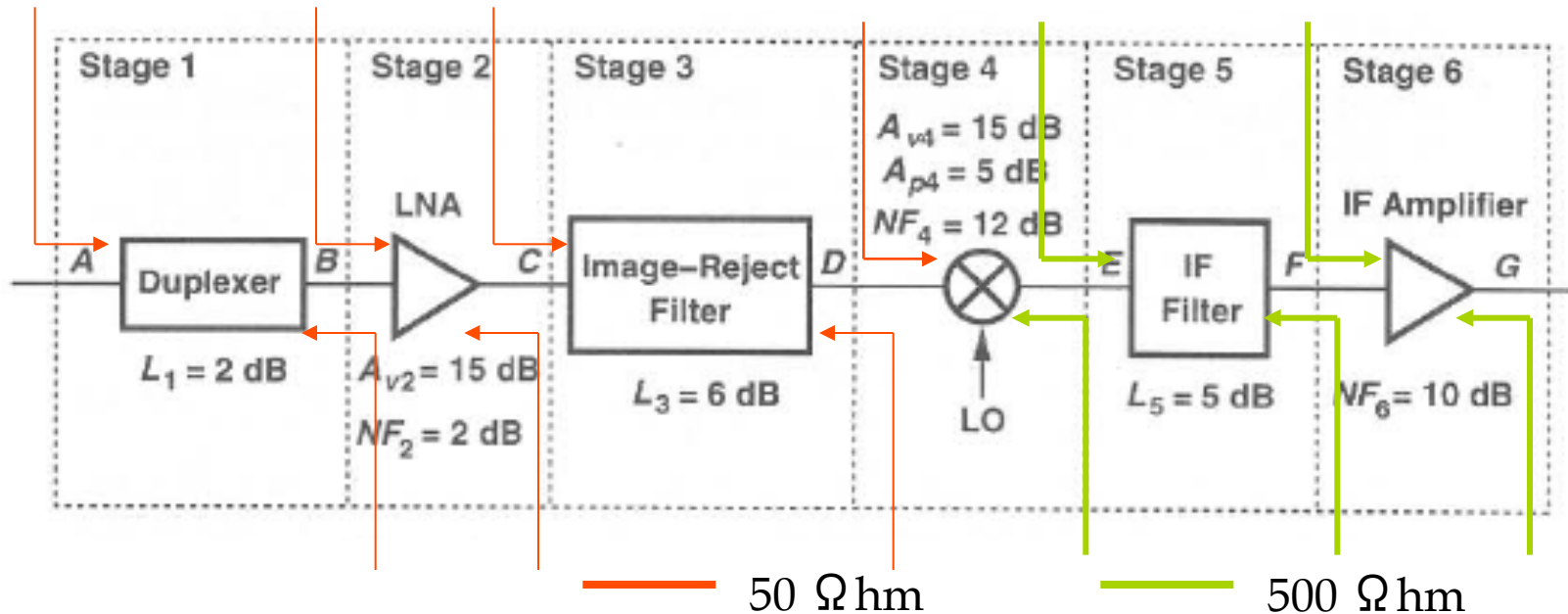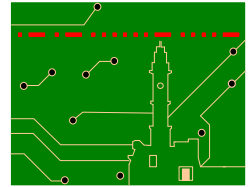

IP3: +100dBm -12dBm +100dBm +5dBm 1000Vrms 700mVrms

- What is the overall IP3?
- Stage input/output not necessarily in 50Ω \Rightarrow use (RMS) voltage gain.
- Passive filters have tremendously large IP3.

Receiver Front End - revisited

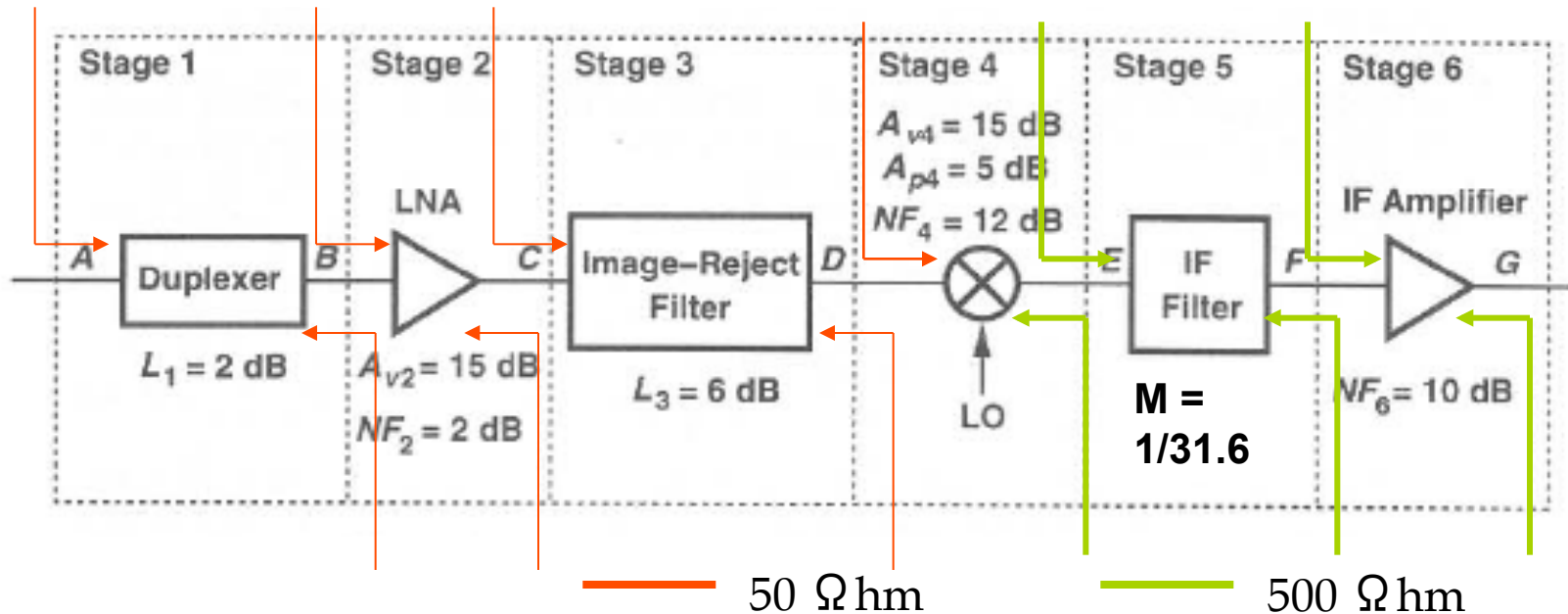
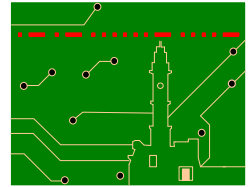


IP3: +100dBm -12dBm +100dBm +5dBm 1000Vrms 700mVrms

$$\frac{1}{IP_{3,E}^2} = \frac{1}{IP_{3,flt}^2} + \frac{M^2}{IP_{3,amp}^2} \approx \frac{M^2}{IP_{3,amp}^2} \Rightarrow IP_{3,E} = \frac{IP_{3,amp}}{M} = 22.1 \text{ Vrms}$$

The voltage gain of stage 5 is $M=1/36$ and is given!

Receiver Front End - revisited

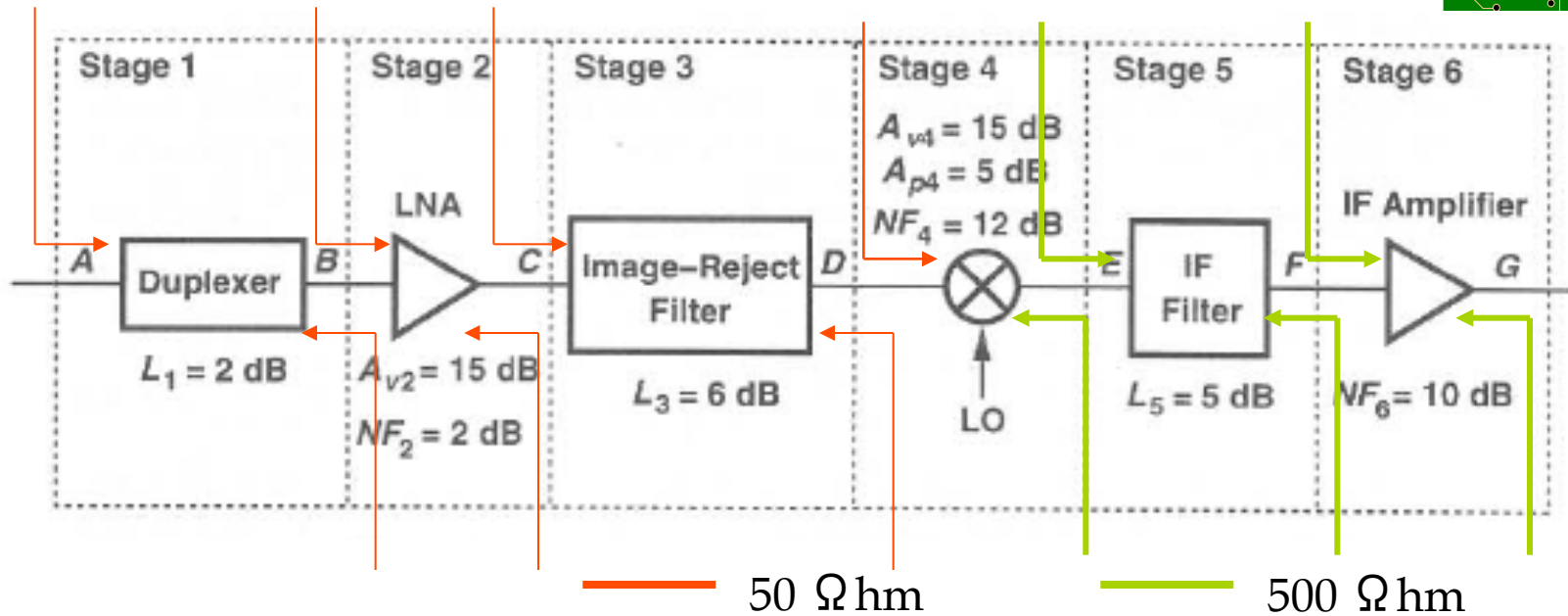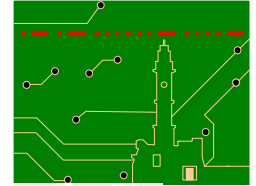


IP3: +100dBm -12dBm +100dBm +5dBm 1000Vrms 700mVrms


$$\frac{1}{IP_{3,D}^2} = \frac{1}{IP_{3,mix}^2} + \frac{A_{v4}^2}{IP_{3,E}^2} = \frac{1}{0.397^2} + \frac{5.62^2}{22.1^2} \approx \frac{1}{0.397^2} \Rightarrow IP_{3,D} = 0.397V_{rms} \approx +5dBm$$

$$IP3 = 5dBm \Rightarrow V_{rms}^2 / 50 = 10^{0.5} mWatt \Rightarrow V_{rms} = 0.397 V_{rms} = 397mV_{rms}$$
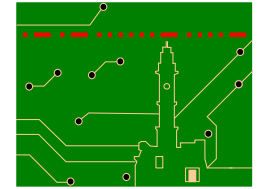
$$A_{v4} = 15 dB \Rightarrow A_{v4} = 10^{15/20} = 5.62$$



Receiver Front End - revisited

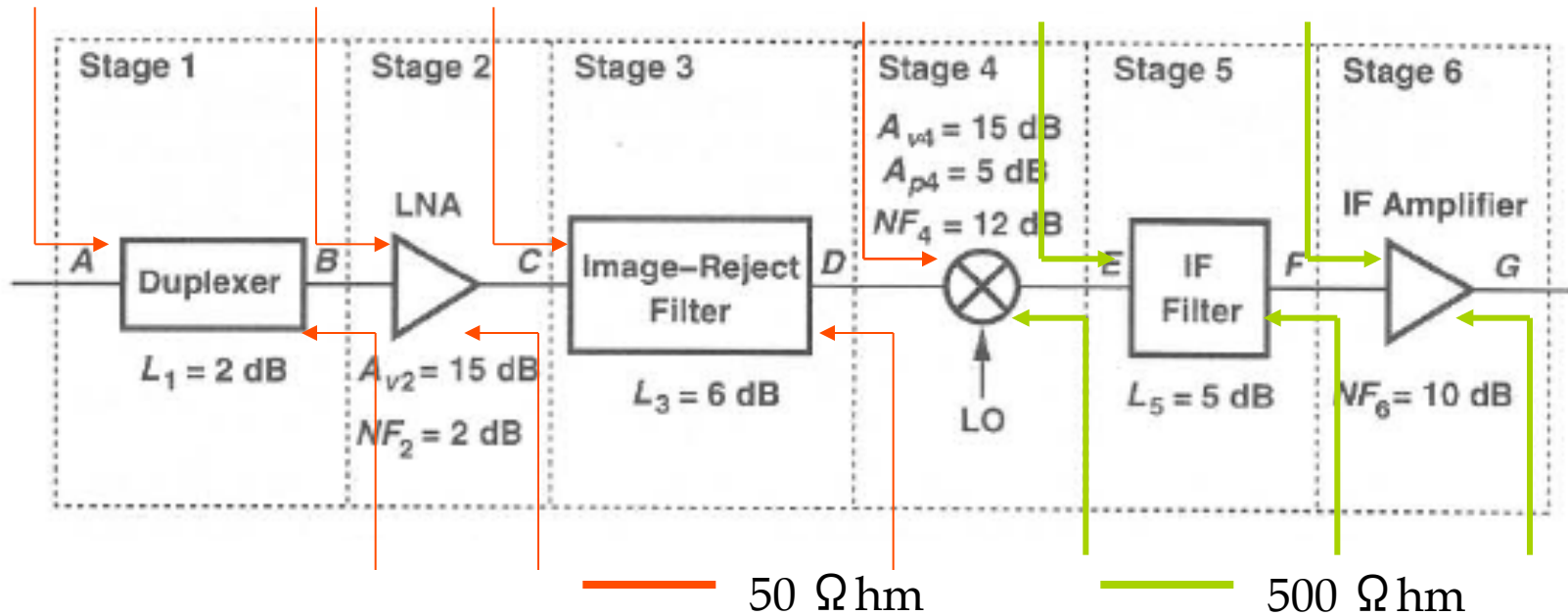


IP₃: +100dBm -12dBm +100dBm +5dBm 1000Vrms 700mVrms
A_v: -2dB +15dB -6dB +15dB (voltage gain)


$$\frac{1}{IP_{3,C}^2} = \frac{1}{IP_{3,flt3}^2} + \frac{A_{v3}^2}{IP_{3,D}^2} \approx \frac{A_{v3}^2}{IP_{3,D}^2} = \frac{0.5^2}{397^2} \Rightarrow IP_{3,C} = 796mVrms \approx +11.03dBm$$

$$A_{v3} = -6 \text{ dB} \Rightarrow A_{v3} = 10^{-6/20} = 0.5$$

Notice that $IP_{3,C} \approx IP_{3,F}$

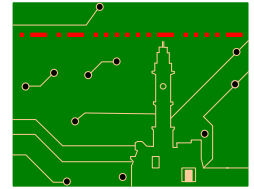

Receiver Front End - revisited

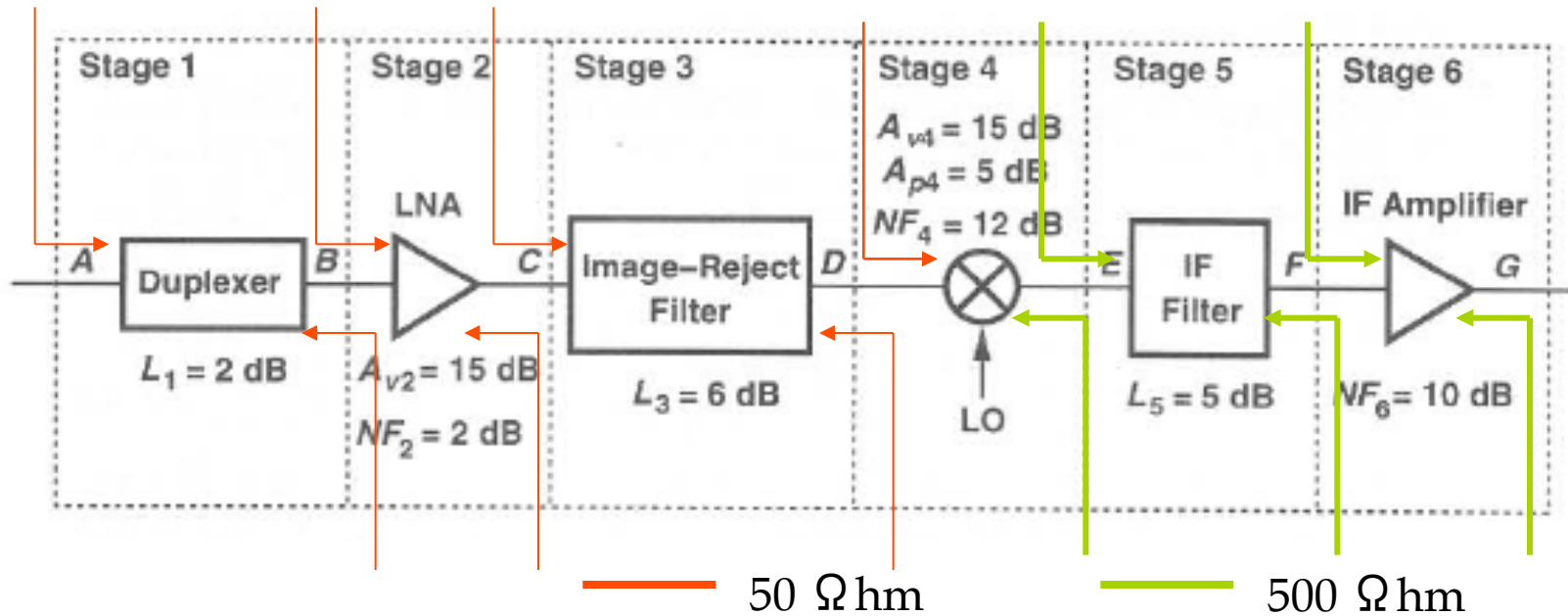

IP3: +100dBm	-12dBm	+100dBm	+5dBm	1000Vrms	700mVrms
A_v : -2dB	+15dB	-6dB	+15dB	(voltage gain)	

➤ Similarly for other two input stages... eventually, $IP_{3,A} = -10.6 \text{ dBm}$

Questions?

